

Code No: 151AG

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD
B.Tech I Year I Semester Examinations, December – 2019/January - 2020
BASIC ELECTRICAL ENGINEERING

(Common to EEE, CSE, IT, IEE)

8R 8R 8R 8R 8R 8R 8R
Time: 3 hours **Max. Marks: 75**

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b as sub questions.

8R 8R 8R 8R 8R 8R 8R
PART - A **(25 Marks)**

- 1.a) What are the initial conditions? [2]
- b) Define the RMS value. [2]
- c) What are the ideal properties of transformer? [2]
- d) Define synchronous speed. [2]
- e) What are the merits of fuse? [2]
- f) State the Thevenin's theorem. [3]
- g) What are the merits of polyphase system? [3]
- h) Draw the different 3-phase transformers connections. [3]
- i) What is the purpose of dampers in a synchronous generator? [3]
- j) What is the need of power factor improvement? [3]

8R 8R 8R 8R 8R 8R 8R
PART - B **(50 Marks)**

- 2.a) Explain the Kirchoff's current and voltage laws.
- b) For the circuit as shown in following figure 1, calculate the current in the various branches? (All resistances are in ohms). [5+5]

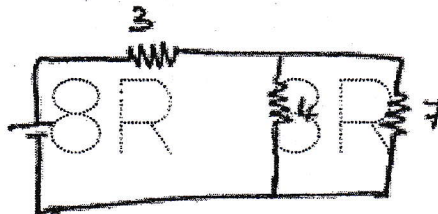


Figure: 1
OR

- 3.a) A Series R-L circuit is supplied by DC voltage. Determine the expression for $i(t)$ when the switch is closed at $t=0$.
- b) Using superposition theorem, find the current through the 8Ω resistor, as shown in below figure 2. [5+5]

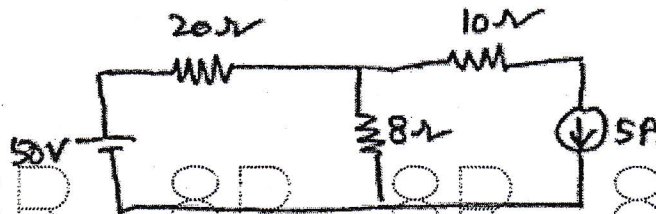


Figure: 2

8R 8R 8R 8R 8R 8R 8R

4.a) Define the following terms:

- i) Frequency
- ii) Peak factor
- iii) Form factor
- iv) Average value of an alternating quantity.

8R

b) A series RLC circuit consists of $R=3$ ohm, $L=2$ mH and $C=0.4$ μ F. Determine the resonant frequency. [5+5]

OR

5.a) Derive the relation between line and phase quantities of voltage and current for a delta system.

b) Determine the line currents when a star connected balanced load with an impedance of $(15+j10)$ ohms is connected to 200V, three phase balanced supply in positive sequence. [5+5]

8R

6.a) From the fundamentals, derive the expression for the EMF equation of a single phase transformer.

b) A 50 kVA, single phase transformer has 500 turns on the primary and 200 turns on the secondary. The primary is connected to 2000V, 50 Hz Supply. Determine: i) The secondary voltage and ii) The maximum value of flux. [5+5]

OR

8R

7.a) What is a transformer? How does it transfer electrical energy from one circuit to another?

b) The primary and secondary voltage of an autotransformer are 500V and 400V respectively. Determine the economy in copper. [5+5]

8.a) Explain the principle of operation of 3-Phase induction Motor.

b) A 10-pole, 3-phase induction motor runs at a speed of 485 rpm at 50 Hz supply. Determine i) synchronous speed and ii) slip. [5+5]

8R

9. Explain the working principle of synchronous generator. [10]

10.a) How the cables/ wires are classified and list out.

b) What are the advantages of earthing? [5+5]

OR

11. What are the types of batteries? Explain. [10]

8R

---00000---

8R

8R