

Code No: 154AW

R18

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech II Year II Semester Examinations, July/August - 2021

ELECTRONIC CIRCUIT ANALYSIS

(Common to ECE, EIE)

Time: 3 Hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

- 1.a) Derive the expression for the bandwidth of multistage amplifier.
- b) What is the use of transformer coupling in the output of multistage amplifier? Give its advantages and disadvantages. [8+7]
- 2.a) Show that bandwidth increases in negative feedback amplifiers.
- b) An amplifier has an input resistance of 200 K ohms, with a certain negative feedback introduced in the above amplifier the input resistance is found to be 20 M ohms and overall gain is found to be 1000. Calculate the loop gain and feedback factor. [8+7]
- 3.a) Derive the expression for frequency of oscillation of Hartley oscillator.
- b) Discuss about Frequency and amplitude stability of oscillators. [9+6]
- 4.a) Describe the operation of Class B Push pull amplifier and show how even harmonics are eliminated.
- b) Derive the expression for conversion efficiency of class-B amplifier. [10+5]
- 5.a) Draw the neat diagram of monostable multivibrator using external connection and explain it in detail.
- b) Determine the frequency of oscillation for the astable multivibrator using IC-555. Given that $R_A=R_B=1K\Omega$ and $C=1000PF$. [10+5]
- 6.a) Discuss in detail about the Validity of hybrid- π model. Also give typical values of hybrid- π conductance and capacitances.
- b) Draw the four types of feedback amplifiers and explain them briefly. [7+8]
- 7.a) Establish the condition for frequency of oscillation in an RC phase shift oscillator.
- b) Derive the expression for maximum conversion efficiency for a Transformer coupled Class A power amplifier. [10+5]
- 8.a) With the help of a neat circuit diagram, explain the working of a simple current sweep.
- b) What are the techniques used to improve the Linearity of current sweeps? Explain. [8+7]