

R15

Code No: 126ZJ

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech III Year II Semester Examinations, July/August - 2021

STATIC DRIVES

(Electrical and Electronics Engineering)

Max. Marks: 75

Time: 3 hours

Answer any five questions
All questions carry equal marks

- 1.a) Explain speed-torque characteristics of a single phase fully controlled converter connected to separately excited D.C. motor with continuous current operation. Draw the relevant waveforms.
- b) The speed of a 50kW, 500V, 120A, 1500 rpm separately excited d.c. motor is controlled by a three phase full converter fed from 400V, 50Hz supply. Motor armature resistance is 0.1Ω . Find the range of firing angle required to obtain speeds between 1000 rpm and (-1000) rpm at rated torque. [8+7]
- 2.a) Explain the speed-torque characteristics of a dc series motor connected to a three phase semi controlled converter.
- b) A series motor is supplied from a full converter whose $\alpha=65^\circ$, 1- ϕ supply of 230 V, 50Hz frequency. The armature and field resistance together equal 2Ω . The torque constant M_{af} is 0.23 H and the load torque is 20 N-m. Neglect damping and find the average armature current and speed. [8+7]
3. With neat circuit diagram and waveforms, explain dynamic braking, regenerative braking and plugging of separately excited motor. [15]
4. Explain the four quadrant operation of D.C motors by dual converters. [15]
- 5.a) Explain principle of operation of two quadrant chopper fed dc series motor. [7+8]
- b) Explain closed loop control of DC motors by choppers.
- 6.a) Describe four quadrant chopper fed dc separately excited motor.
- b) Draw and explain output voltage and current waveforms of chopper fed dc separately excited motor. [7+8]
- 7.a) Write short notes on static Kramer drive. [8+7]
- b) Explain principle of operation of static scherbius drive.
8. Describe the open-loop and closed loop methods of speed control of a synchronous motor using VSI. [15]

---ooOoo---