

Code No.: EE204ES

R20

H.T.No.

8 R

CMR ENGINEERING COLLEGE: : HYDERABAD
UGC AUTONOMOUS
I-B.TECH-II-Semester End Examinations (Supply) - January- 2022
BASIC ELECTRICAL ENGINEERING
(Common to CSM, ECE)

[Time: 3 Hours]

[Max. Marks: 70]

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 20 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART-A


(20 Marks)

1. a) Define Capacitance and write the expression for voltage across a capacitor. [2M]
- b) State Thevenin's Theorem. [2M]
- c) Define the terms Impedance and Reactance. [2M]
- d) Draw the phasor diagram of a series RC circuit. Also define power factor. [2M]
- e) List the various losses in a Transformer. [2M]
- f) Mention the properties of an ideal Transformer. [2M]
- g) What is the significance of back EMF in DC motor? [2M]
- h) List the classification of various DC generators. [2M]
- i) Mention different starting methods used in three-phase induction motor. [2M]
- j) Write the significance of rotating magnetic field in the operation of three-phase Induction Motor. [2M]

PART-B

(50 Marks)

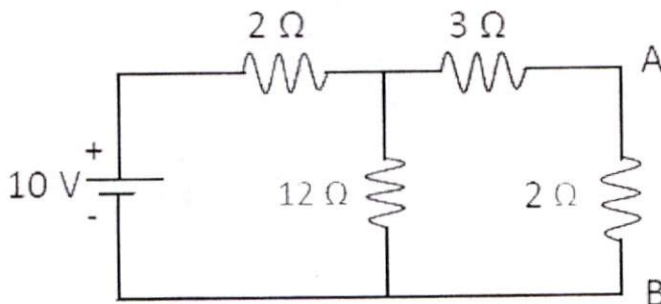2. A Series RC circuit is supplied by DC voltage. Determine the expression for $i(t)$ when the switch is closed at $t=0$. [10M]
- OR**
3. Determine the current through 2Ω resistor connected between the terminals AB using Norton's theorem. Also draw its equivalent circuit. [10M]



4. Derive the expressions for RMS value and Average value of a sinusoidal quantity. Also show that form factor of sinusoidal alternating current wave is 1.11. [10M]
- OR**
5. a) A $20\text{-}\Omega$ resistor, 20-mH inductor and $20\text{-}\mu\text{F}$ capacitor are connected in series with a 20-kHz voltage source. The RMS current through the circuit is 0.30 A . Find the RMS voltage drop across each of the elements. [5M]
 - b) Derive the voltage and current relationships in a Three-phase balanced delta connected network. [5M]
6. Describe various three phase transformer connections and their significance? [10M]

OR

7. a) Draw the equivalent circuit of a single-phase Transformer and explain each part in it. [6M]
b) Derive the condition for maximum efficiency in a Transformer. [4M]

8. a) A shunt wound DC generator delivers 10 A at 220 V to a load. The resistance of the shunt field coil is 100Ω and that of the armature winding 0.02Ω . Calculate the EMF induced in the armature. [5M]
b) Derive the EMF equation of a DC Generator. [5M]

OR

9. Draw and explain the performance characteristics of a DC Shunt and Series Motors. [10M]

10. Describe the construction and working of Synchronous Generator. [10M]

OR

11. Derive the expression for torque in a three-phase Induction Motor. Also explain Torque-Slip characteristics. [10M]
