

Code No.: EC302PC

R20

H.T.No.

8

R

**CMR ENGINEERING COLLEGE: : HYDERABAD  
UGC AUTONOMOUS**

**II-B.TECH-I-Semester End Examinations (Regular) - January- 2022  
DIGITAL SYSTEM DESIGN  
(ECE)**

[Time: 3 Hours]

[Max. Marks: 70]

**Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 20 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

**PART-A**

**(20 Marks)**

1. a) Convert  $(1010110110.1011011)_2$  to Octal and Hexadecimals. [2M]
- b) Draw the Logic symbol and construct the truth table for Three Input OR gate. [2M]
- c) What is a standard POS form? [2M]
- d) What is Hazard? [2M]
- e) In a 6-bit Johnson Counter sequence there are a total of how many States, or Bit patterns? [2M]
- f) What is meant by Race around condition in Flip Flops? [2M]
- g) By how many models are Synchronous sequential circuits represented? Name them. [2M]
- h) What is a Twisted Ring Counter? [2M]
- i) What are the characteristics of Logic families? [2M]
- j) What is TTL and CMOS logic? [2M]

**PART-B**

**(50 Marks)**

2. What is Parity Checking? Explain its necessity and implementation? [10M]
- OR**
3. Draw the circuit diagrams for each of the following. How can a (i) NAND be used as an Inverter (ii)NOR be used as an Inverter (iii) NOR be used as OR (iv) NAND be used as AND (v) NAND be used as NOR [10M]
4. Simplify the Boolean function using K-map in SOP and POS forms [10M]  
 $F = \sum m(0,1,2,4,7,8,12,14,15,16,17,18,20,24,28,30,31)$ .
- OR**
5. Implement the Full adder using 3-line to 8-line Decoder. [10M]
6. Define the following terms with relation to Flip Flop (i)Setup Time(ii)Hold Time(iii)Propagation Delay Time(iv)Present State(v)Clear State. [10M]
- OR**
7. Construct a T Flip Flop from a JK Flip Flop and explain its Truth Table. [10M]
8. Design a Synchronous mod-6 Counter using JK-Flip Flops. [10M]
- OR**
9. Design XS3 to BCD Code Converter using a (i) PROM (ii) PLA and (iii) PAL. [10M]
10. What is significance of Logic families and also mention the types of Logic families? [10M]
- OR**
11. Construct an exclusive NOR circuit using Transmission Gates and Inverters. [10M]

\*\*\*\*\*