

Code No.: EC301PC

R20

H.T.No.

8 R

**CMR ENGINEERING COLLEGE: : HYDERABAD**  
**UGC AUTONOMOUS**  
**II-B.TECH-I-Semester End Examinations (Regular) - January- 2022**  
**ELECTRONIC DEVICES AND CIRCUITS**  
**(ECE)**

[Time: 3 Hours]

[Max. Marks: 70]

**Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 20 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub-questions.

**PART-A**

(20 Marks)

1. a) Define diffusion and transition capacitance of p-n junction diode. [2M]
- b) Distinguish clippers and clampers circuits with figures. [2M]
- c) Obtain the condition for thermal stability of a BJT used in a biasing circuit? [2M]
- d) Describe thermal stability. [2M]
- e) Draw and explain Zener diode characteristics. [2M]
- f) Justify the statement "input impedance of FET is higher than BJT" [2M]
- g) Discuss briefly the advantages of h-parameter for analysis of amplifiers. [2M]
- h) Summarize the low frequency response of BJT amplifier. [2M]
- i) Explain the JFET Small signal Model. [2M]
- j) Analyze the MOSFET characteristics in enhancement mode with required diagrams. [2M]

**PART-B**

(50 Marks)

2. List different part of V-I characteristics of a diode and also draw V-I characteristics of a PN diode [10M]  
for the following conditions:
  - i)  $R_f = 0, V_\gamma = 0, R_r = \infty$
  - ii)  $R_f = 0, V_\gamma = 0.6V, R_r = \infty$
  - iii)  $R_f = \text{Non-zero, fixed value}, V_\gamma = 0, R_r = \infty$
  - iv)  $R_f = \text{Non-zero, fixed value}, V_\gamma = 0.6V, R_r = \infty$Where  $V_\gamma$  is the cut-in voltage,  $R_f$  is the forward dynamic resistance &  $R_r$  is the reverse dynamic resistance of the diode.

**OR**

3. With reference to the rectifiers, explain the following terms and mention its values to different types of rectifiers: [10M]
  - i) Ripple Factor
  - ii) Efficiency
  - iii) Peak Inverse Voltage (PIV)
  - iv) % Regulation
4. Define Early-effect, justify why it is called as base-width modulation, and discuss its consequences in transistors in detail? [10M]

**OR**

5. a) Illustrate the circuit diagram of the NPN transistor in the Common Emitter (CE) configuration. [5M]
- b) With neat sketches and necessary equations, describe its input-output characteristics and clearly indicate the cut-off, saturation & active regions on the output characteristics? [5M]

6. With a neat sketch, discuss about common source FET amplifier, and explain, how FET is working as Voltage Variable Resistor? [10M]

OR

7. Explain the construction of FET and the principle of operation. Also compare the characteristics of FET with BJT [10M]


8. a) Draw and discuss the circuit diagram & small-signal equivalent of CB amplifier using the accurate h-parameter model. [5M]

b) Derive expressions for  $A_v$ ,  $A_i$ ,  $R_i$  and  $R_o$  [5M]

OR

9. Analyze the small-signal equivalent circuit of Emitter Follower using accurate h-parameter model. For the emitter follower circuit with  $R_s = 0.5\text{K}$  and  $R_L = 5\text{K}$ , Compute  $R_i$ ,  $A_v$  and  $R_o$ . Assume,  $h_{fe} = 50$ ,  $h_{re} = 1$ ,  $h_{oe} = 25\ \mu\text{A/V}$  and  $h_{ie} = 1.1\text{K}$ . [10M]

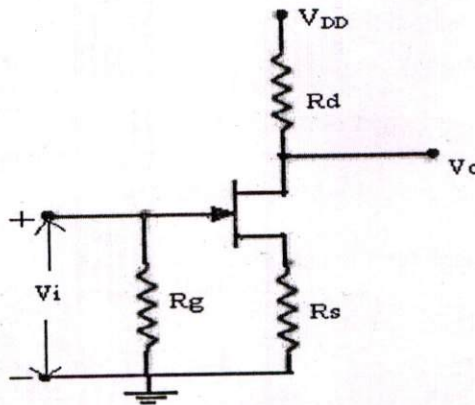10. A Common Source FET amplifier circuit shown in Figure with un-bypassed  $R_s$  has the following circuit parameters:  $R_d = 15\text{K}$ ,  $R_s = 0.5\text{K}$ ,  $R_g = 1\text{M}$ ,  $r_d = 5\text{K}$ ,  $g_m = 5\text{mS}$  and  $V_{DD} = 20\text{V}$ . Calculate  $R_i$ ,  $A_v$  and  $R_o$  [10M]



OR

11. List the different types of MOSFETs, discuss the differences between the construction & operation of a N-channel MOSFET in enhancement and depletion modes with diagrams [10M]

\*\*\*\*\*