

Code No.: EC403PC

R20

H.T.No.

		8	R						
--	--	---	---	--	--	--	--	--	--

CMR ENGINEERING COLLEGE: : HYDERABAD
UGC AUTONOMOUS
II-B.TECH-II-Semester End Examinations (Regular) - June- 2022
LINEAR IC APPLICATIONS
(ECE)

[Time: 3 Hours]

[Max. Marks: 70]

- Note:** 1. Answer any FIVE questions. Each question carries 14 marks.
2. All questions carry equal marks.
3. Illustrate your answers with NEAT sketches wherever necessary.

5X14=70

1. a) For Op-amp, CMRR = 10^5 and differential mode gain $A_{DM} = 10^5$. Calculate the common mode gain A_{CM} of the Op-amp. [7M]
b) With block diagram, explain the general stages of an Op -Amp IC. [7M]
2. a) Draw a sample and hold circuit. Explain its operation and indicate its uses. [7M]
b) Explain the difference between the integrator and differentiator and give one application of each. [7M]
3. a) Design a HPF at a cut-off frequency of 1 kHz and pass band gain of 2. [7M]
b) With circuit diagram, describe the working of a Wien bridge oscillator circuit using op -amp. [7M]
4. a) The free running frequency of a 565 PLL is 100 kHz, the filter capacitor is $2\mu\text{F}$ and supply voltage is $\pm 6\text{V}$. Compute the lock in range, capture range frequency and value of external components R_T and C_T . [7M]
b) A 555 timer Astable multivibrator uses $R_A = 6.8\text{ k}\Omega$, $R_B = 3.3\text{ k}\Omega$ and $C = 0.1\ \mu\text{F}$. Calculate the free running frequency of oscillation. [7M]
5. a) Determine the output voltages caused by each bit in a 6-bit ladder if the input levels are $0=0\text{V}$ and $1=+16\text{V}$. Determine the resolution and full-scale output of this circuit. Find out the voltage from the above ladder for a digital input of 101011. [7M]
b) Draw the circuit and explain the working of dual slope A/D converter. [7M]
6. a) Define Slew rate. How it effect the op-amp performance? Explain. [7M]
b) Sketch the equivalent circuit of an Op-amp & Define common mode rejection ratio. [7M]
7. a) Draw the circuit of (i) voltage to current (V to I) converter with grounded load (ii) current to voltage (I to V) converter with grounded load. [7M]
b) Sketch an adder circuit using op -amp to obtain the sum of three inputs. [7M]
8. a) What is the relationship between order of a filter and roll off rate? [7M]
b) Why do we use higher order filters and List the applications of VCO. [7M]
