

Code No.: EC401PC

R20

H.T.No.

8

R

CMR ENGINEERING COLLEGE: : HYDERABAD
UGC AUTONOMOUS

II-B.TECH-II-Semester End Examinations (Regular) - June- 2022
NETWORK ANALYSIS AND TRANSMISSION LINES
(ECE)

[Time: 3 Hours]

[Max. Marks: 70]

- Note:** 1. Answer any *FIVE* questions. Each question carries 14 marks.
2. All questions carry equal marks.
3. Illustrate your answers with NEAT sketches wherever necessary.

5X14=70

1. a) What is a basic Cutset Matrix? Explain with an example. [7M]
b) Draw the T equivalent model for magnetically coupled circuits and explain. [7M]
2. a) What is the damping factor? Explain the step response of the second-order system with a underdamped case. [7M]
b) Determine quality factor and bandwidth for the parallel RLC resonant circuit. Given $R = 100 \Omega$, $L = 0.2 \text{ mH}$ and $C = 500 \mu\text{F}$. [7M]
3. a) Explain different parameters to be considered for the design of attenuators. [7M]
b) Draw the symmetrical T and π sections and their decomposition into L sections. [7M]
4. a) Calculate the characteristic impedance for the following line parameters: $R = 10.4 \text{ ohms/km}$; $L = 0.00367 \text{ H/km}$; $C = 0.00835 \mu\text{F/km}$ and $G = 10.8 \times 10^{-6} \text{ mhos/km}$ [7M]
b) Derive the primary constants (R, L, C, and G) of an infinite transmission line. [7M]
5. A transmission line has an impedance of 300Ω is terminated with the load impedance of $150 + j150 \Omega$ then determine the following parameters using Smith chart. i) VSWR ii) Reflection Coefficient iii) input impedance at 0.1λ distance from the load. iv) Input admittance at 0.1λ distance. v) Voltage minimum and maximum. [14M]
6. a) What is an electric circuit? What is a magnetic circuit? Make a comparison between the electric circuit and the magnetic circuit. [7M]
b) A Coil 1 of a pair of coupled coils has a continuous current of 5A, and the corresponding fluxes ϕ_{11} and ϕ_{12} are 0.2 and 0.4 mWb respectively. If the turns are $N_1 = 500$ and $N_2 = 1500$, find L_1 , L_2 , M, and k. [7M]
7. a) Derive and draw the response of a series RLC circuit for a step input. [7M]
b) An impedance $Z_1 = 10 + j10 \Omega$ is connected in parallel with another impedance of resistance 8.5Ω and a variable capacitance connected in series. Find C such that the circuit is in resonance at 5 kHz. [7M]
8. a) Derive the characteristics impedance of π section network. [7M]
b) Define Hybrid parameters of a Two Port network. Establish the relation between Hybrid Parameters and ABCD Parameters. [7M]
