

Code No.: EE104ES

R22

H.T.No.

8

R

CMR ENGINEERING COLLEGE: : HYDERABAD
UGC AUTONOMOUS

I-B.TECH-I-Semester End Examinations (Regular) - March- 2023
BASIC ELECTRICAL ENGINEERING
(Common for CSC, CSD, CSM)

[Time: 3 Hours]

[Max. Marks: 60]

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 10 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART-A


(10 Marks)

1. a) What is inductance? [1M]
- b) State KCL. [1M]
- c) Define r.m.s value of a sinusoidal waveform. [1M]
- d) Give the relation between line and phase quantities of 3-phase star connection. [1M]
- e) What is an Ideal transformer? [1M]
- f) Give the condition for maximum efficiency of a transformer. [1M]
- g) What is the function of commutator in d.c generator? [1M]
- h) Give the expression for torque of a d.c motor. [1M]
- i) Define slip. [1M]
- j) State various types of 3-phase Induction motors. [1M]

PART-B

(50 Marks)

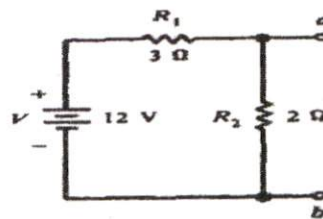2. a) State and explain Norton's theorem. [5 M]
- b) Find the Thevenin's equivalent circuit across a, b terminals of the circuit shown below. [5 M]



OR

3. a) State and explain superposition theorem. [5 M]
 - b) Discuss the transient current growth in an series R-L circuit excited by d.c source. [5 M]
 4. a) Explain (i) active power (ii) reactive power [4 M]
 - b) A RL series ac circuit has a current of 1 A peak with $R = 500 \Omega$ and $X_L = 50 \Omega$. Calculate V_R , V_L , V_T , and θ . Draw the phasor diagram of V_T and I . [6 M]
- OR
5. a) Derive an expression for resonant frequency of R-L-C series circuit excited by a.c source. [5 M]
 - b) 20- Ω resistor and a 15 Ω inductive reactance are placed in parallel across a 120-V ac. Find the branch currents and the total current, [5 M]

6. a) Explain various losses that are occurred in a single phase transformer. [6 M]
 b) A single phase transformer reduces the 120 V in the primary to 8 V on the secondary. [4 M]
 If there are 150 turns on the primary and 10 turns on the secondary, find the voltage ratio and turns ratio.

OR

7. a) Obtain the equivalent circuit of transformer. [5 M]
 b) A 250-KVA, 2400/480-V transformer has copper losses of 3760 W and core losses of 1060 W. What is the efficiency when the transformer is fully loaded at 0.8 power factor? [5 M]

8. a) Derive an e.m.f equation of a d.c generator. [5 M]
 b) Explain the working principle of d.c motor. [5 M]

OR

9. a) Draw the torque –speed characteristics of all d.c motors. [5 M]
 b) Find the back emf of a motor when the terminal voltage is 240V and the armature current is 50 A. The armature resistance is 0.08 Ω. The field current is negligible. [5 M]
 What is the power developed by the motor armature?

10. Explain the constructional details and working principle of 3-phase induction motor. [10M]

OR

11. Why starter is needed for 3-phase Induction Motor? Explain the operation of star-delta starter with a neat circuit diagram. [10M]

