

Code No.: EC301PC

R20

H.T.No.

8 R

CMR ENGINEERING COLLEGE: : HYDERABAD
UGC AUTONOMOUS

II-B.TECH-I-Semester End Examinations (Regular) - February- 2023
ELECTRONIC DEVICES AND CIRCUITS
(ECE)

[Time: 3 Hours]

[Max. Marks: 70]

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 20 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART-A

(20 Marks)

1. a) Define Static and Dynamic resistance levels of diode. [2M]
- b) Compare Drift and Diffusion currents of semiconductor. [2M]
- c) Define current amplification factors (α, β, γ). [2M]
- d) Explain how transistor acts as an Amplifier. [2M]
- e) Why the input impedance of FET is higher than BJT. [2M]
- f) Compare BJT and FET transistors. [2M]
- g) Draw BJT transistor small signal low frequency hybrid model. [2M]
- h) Define input impedance (Z_i) and output impedance (Z_o) of a transistor. [2M]
- i) Draw the H-Parameter model circuit for CB configuration. [2M]
- j) Define transconductance (g_m) and drain resistance(r_d) of a FET. [2M]

PART-B

(50 Marks)

2. a) Draw and explain V-I characteristics of PN junction diode. [5M]
 - b) Explain simple clipper and clamper circuits with circuit diagram. [5M]
- OR**
3. A Half wave rectifier has a load of 3.5 K Ω . If the diode resistance and the secondary coil resistance together have a resistance of 800 Ω and the input voltage has a signal voltage of 240 V, calculate [10M]
 - i) Peak, average and RMS value of current flowing.
 - ii) DC power output.
 - iii) AC power input
 - iv) Efficiency of the rectifier.
4. a) Differentiate between NPN and PNP transistors. [5M]
 - b) List out Few comparisons of CB, CE and CC configurations with examples. [5M]
- OR**
5. a) Draw the circuit diagram of a PNP junction transistor in CE configuration and describe its characteristics. [5M]
 - b) Draw and explain the Fixed Bias Circuit. [5M]

6. a) Explain the construction and operation of N-channel JFET. [5M]
b) Draw and explain the drain and transfer characteristics of N-channel JFET. [5M]
- OR**
7. Discuss the operation and characteristics of the following: [5M]
a) SCR [5M]
b) UJT
8. Draw and explain the H-Parameter equivalent circuit of a transistor in CC configuration. Derive the expressions for input impedance, output impedance and voltage gain. [10M]
- OR**
9. For a Common Emitter (CE) circuit draw the H-Parameter equivalent circuit and write the expressions for input impedance, output impedance and voltage gain. [10M]
10. Explain MOSFET characteristics in Enhance mode and Depletion mode. [10M]
- OR**
11. Draw the small signal equivalent circuit of JFET amplifier in CS connection and derive the equations for voltage gain, input impedance and output impedance. [10M]
