

Code No.: EC301PC

R20

H.T.No.

8

R

CMR ENGINEERING COLLEGE: : HYDERABAD
UGC AUTONOMOUS
II-B.TECH-I-Semester End Examinations (Supply) - August- 2023
ELECTRONIC DEVICES AND CIRCUITS
(ECE)

[Time: 3 Hours]

[Max. Marks: 70]

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 20 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART-A

(20 Marks)

1. a) Write the expression for transition capacitance (C_T) of a PN junction diode. [2M]
- b) Define transconductance (g_m) and drain resistance (r_d) of a FET. [2M]
- c) Explain the following terms with reference to a BJT [2M]
 - i. Emitter transportation factor (β).
 - ii. Base transportation factor (α).
- d) Explain how transistor bias compensation using diode is useful, list its advantages. [2M]
- e) List the applications of FET. [2M]
- f) Draw the characteristics of SCR. [2M]
- g) Briefly explain the effect of coupling and bypass capacitor on CE amplifier. [2M]
- h) Compare CB, CE, CC configurations in terms of input and output resistances. [2M]
- i) Justify the statement "A depletion mode MOSFET can also be operated in enhancement mode but an enhancement mode MOSFET cannot be operated in depletion mode". [2M]
- j) Draw the circuit diagram of fixed bias arrangement of a JFET. [2M]

PART-B

(50 Marks)

2. With neat sketches discuss the operation of a Full Wave Rectifier with L- section filter & derive the expression for its ripple factor. [10M]
- OR**
3. a) Explain PN junction diode characteristics in forward bias and reverse bias regions. [5M]
 - b) Compare the different parameters of half wave, full wave and bridge rectifier with diagrams. [5M]
4. With a neat diagram explain the various current components in an NPN bipolar junction transistor & hence derive general equation for collector current I_C . [10M]
- OR**
5. Draw the circuit diagram of NPN transistor in Common Base (CB) configuration and explain with its characteristics. [10M]
6. With neat energy band diagrams, explain the V-I characteristics of Tunnel diode. Also discuss the negative resistance property of tunnel diode. [10M]
- OR**
7. Draw the basic structure and equivalent circuit of UJT, and also explain how the UJT can be used as a negative-resistance device with the aid of static characteristics. [10M]

8. Find the values of A_v , A_i , R_i and R_o for a bipolar junction transistor with $h_{ie} = 1100\Omega$, $h_{re} = 50$, $h_{re} = 2.4 \times 10^{-4}$, $h_{oe} = 25 \mu A/V$, is to drive a load of $1K\Omega$ in CB amplifier arrangement. [10M]

OR

9. Compare CB, CE and CC amplifiers in terms of A_v , A_i , R_i and R_o . [10M]
10. Explain the construction & operation of a N-channel MOSFET in enhancement and depletion modes with the help of static drain characteristics and transfer characteristics. [10M]

OR

- 11.a) Compare CS, CD and CG configurations of FET amplifiers. [5M]
- b) Explain the varactor diode with neat diagram. [5M]
