

Code No.: EC57202PC

R20

H.T.No.

8 R

CMR ENGINEERING COLLEGE: : HYDERABAD
UGC AUTONOMOUS
I-M.TECH-II-Semester End Examinations (Regular) - September- 2022
LOW POWER SYSTEM DESIGN
(VLSI System Design)

[Time: 3 Hours]

[Max. Marks: 70]

- Note:** 1. Answer any FIVE questions. Each question carries 14 marks.
2. All questions carry equal marks.
3. Illustrate your answers with NEAT sketches wherever necessary.

5X14=70

- | | | |
|-------|--|------|
| 1. a) | Analyze the effects of V_{DD} and V_T on speed. | [8M] |
| b) | Describe the impact of technology scaling. | [6M] |
| 2. a) | Describe the Power consumption in flip-flops and latches. | [7M] |
| b) | Describe the power dissipation in clock distribution. | [7M] |
| 3. a) | Analyze the logic synthesis for low power estimation techniques. | [7M] |
| b) | Discuss Low power arithmetic components of multipliers. | [7M] |
| 4. a) | Explain the concept of Low-Power Memory design? | [7M] |
| b) | Discuss the sources of power dissipation in SRAM. | [7M] |
| 5. a) | Compare different microprocessors in terms of power and performance. | [6M] |
| b) | Explain the concepts of low power microprocessor design. | [8M] |
| 6. a) | Describe the sources of power dissipation in digital IC's. | [7M] |
| b) | Discuss recurring themes in low power circuits. | [7M] |
| 7. a) | Explain the different approaches of Low power design at circuit level. | [7M] |
| b) | Discuss the types of energy recovery in CMOS circuits. | [7M] |
| 8. a) | Explain the Low power arithmetic components circuit design styles. | [7M] |
| b) | Discuss briefly about power minimization techniques in low power design. | [7M] |
