

Code No.: EC57202PC

R20

H.T.No.

8

R

CMR ENGINEERING COLLEGE: : HYDERABAD

UGC AUTONOMOUS

I-M.TECH-II-Semester End Examinations (Supply) - Feb- 2022

LOW POWER SYSTEM DESIGN

(VLSI SD)

[Time: 3 Hours]

[Max. Marks: 70]

**Note:** This question paper contains two parts A and B.  
Part A is compulsory which carries 20 marks. Answer all questions in Part A.  
Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

**PART-A**

(20 Marks)

1. a) Explain the need for low power circuit design? [2M]
- b) What are the limitations of low power designing? [2M]
- c) Write about Pipelining method for low power circuit design? [2M]
- d) Write a short note on low power dissipation measures? [2M]
- e) Write about the classification of multipliers? [2M]
- f) What is the effect of feature scaling on power dissipation? [2M]
- g) Write a note on MASK level measures for low power circuit design? [2M]
- h) What are the different low power techniques for SRAM? [2M]
- i) List various low power design techniques for microprocessors? [2M]
- j) What is resonant clocking? [2M]

**PART-B**

(50 Marks)

2. What are the various limitations of low voltage low Power design? Explain? [10M]
3. With neat sketches, Explain variable threshold CMOS inverter circuit? [10M]
4. a) Describe static and semi-static flip flops with neat diagrams? [5M]
- b) Define clock skew? How clock skew is calculated in timing analysis? [5M]
5. Explain the need for Low-power latches and flip flops? [10M]
6. With the neat diagrams explain about Booth multiplier? [10M]
7. Explain the different configurations of full adder circuit? [10M]
8. a) Show the differences between DRAM and SRAM? [4M]
- b) Discuss low power SRAM circuits with neat diagrams. [6M]
9. Analyze the various techniques at architectural level used to design low power memories? [10M]
10. Explain implementation problems of low power design systems? [10M]
11. Explain the architectural tradeoffs that need to be considered for choosing power and supply voltage? [10M]

\*\*\*\*\*