

6/2/24

Code No.: R22EC301ES

R22

H.T.No.

8

R

**CMR ENGINEERING COLLEGE: : HYDERABAD**  
**UGC AUTONOMOUS**

**II-B.TECH-I-Semester End Examinations (Regular) - February- 2024**  
**ANALOG & DIGITAL ELECTRONICS**  
**(Common for IT, CSM)**

[Time: 3 Hours]

[Max. Marks: 60]

**Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 10 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

**PART-A****(10 Marks)**

1. a) Draw the piecewise linear volt-ampere characteristic of a p-n diode. [1M]
- b) Define peak inverse voltage. [1M]
- c) What are transistor regions? [1M]
- d) What are the classifications of Multistage amplifiers? [1M]
- e) Draw the symbol of universal gates. [1M]
- f) Draw the CMOS inverter circuit. [1M]
- g) Define Multiplexer. [1M]
- h) Draw 1-bit digital comparator. [1M]
- i) Define a sequential system and how does it differ from a combinational system? [1M]
- j) Define a ROM. [1M]

**PART-B****(50 Marks)**

2. a) Explain V-I characteristics of a PN junction diode. [5M]
  - b) Determine the forward bias voltage applied to silicon diode to cause a forward current of 10mA and reverse saturation current  $I_0=25 \times 10^{-7}$  A at room temperature [5M]
- OR**
3. Explain the action of a full-wave rectifier and give waveforms of input and output voltages. [10M]
  4. What is an amplifier? And explain various types of amplifiers. [10M]
- OR**
5. A CE amplifier is driven by a voltage source of internal resistance  $R_S = 800 \Omega$ , and the load impedance is a resistance  $R_L = 1000 \Omega$ . The h-parameters are  $h_{ie} = 1 \text{ k} \Omega$ ,  $h_{re} = 2 \times 10^{-4}$ ,  $h_{fe} = 50$  and  $h_{oe} = 25 \mu\text{A/V}$ . Compute the current gain  $A_i$ , input resistance  $R_i$ , voltage gain  $A_v$  and output resistance  $R_o$  using exact analysis and using approximate analysis. [10M]
  6. Draw the small signal equivalent circuit of FET amplifier in CS connection and derive the equations for voltage gain, input impedance and output impedance. [10M]
- OR**
7. a) Explain the De Morgan's Laws. [5M]
  - b) Simplify the following Boolean expressions [5M]
    - i.  $A+AB+ABC+ABCD$
    - ii.  $AB+BC+A'C$
  8. Implement full adder with two half adders and an OR gate. [10M]
- OR**
9. Minimize the following Boolean functions using K-map and draw the logic diagram using NAND gates. [10M]
- $F(A,B,C,D) = \sum m(1,3,5,8,9,11,15) + d(2,13)$

10. Convert the S R Flip Flop to T flip Flop. [10M]
- OR**
11. Explain how a shift register is used as a converter from i) serial-to-parallel data and [10M]  
ii) parallel-to-serial data.

\*\*\*\*\*