

Code No.: R22EE104ES

R22

H.T.No.

8 R

CMR ENGINEERING COLLEGE: : HYDERABAD
UGC AUTONOMOUS
I-B.TECH-I-Semester End Examinations (Regular) - February- 2024
BASIC ELECTRICAL ENGINEERING
(Common for IT, CSD, CSM)

[Time: 3 Hours]

[Max. Marks: 60]

Note: This question paper contains two parts A and B.
Part A is compulsory which carries 10 marks. Answer all questions in Part A.
Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART-A


(10 Marks)

1. a) Define ohm's law and write its limitations. [1M]
- b) What is Source transformation technique? [1M]
- c) Define power factor? [1M]
- d) Write the advantages of sine wave in A.C quantities. [1M]
- e) Draw the equivalent circuit of transformer referred to primary. [1M]
- f) Why transformer is rated in KVA? [1M]
- g) List the different types of DC Motors. [1M]
- h) What are the characteristics of DC motors? [1M]
- i) Define Slip of an induction motor. [1M]
- j) Why Induction motor is called rotating transformer? [1M]

PART-B


(50 Marks)

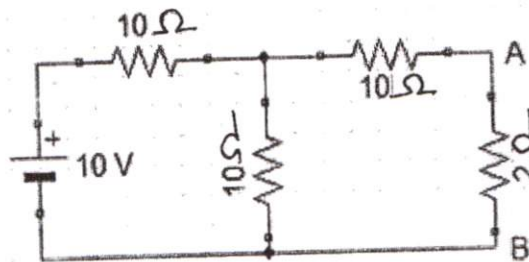2. a) Analyze the V-I relationship between R L C Parameters. [5M]
- b) Apply Thevenin's theorem to find the Thevenin's equivalent circuit between the nodes A-B [5M]



OR

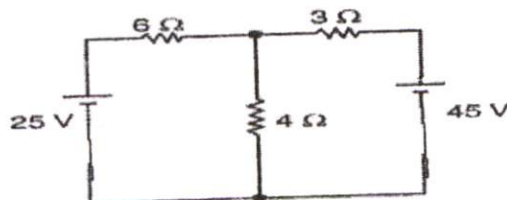3. a) Using Kirchoff's laws, find the current in various resistors in the circuit shown [5M]



- b) State and explain Superposition theorem with an example. [5M]

4. a) Analyse RL Series circuit with necessary diagrams and equations. [5M]
b) A resistance of 30Ω , and a capacitance of $200\mu\text{F}$ are connected in series across a 230V , 50Hz supply. Find (i) Current (ii) Phase angle (iii) Voltage across each element. [5M]
iv) Active and Reactive power.
- OR**
5. a) Define following terms [5M]
i. Instantaneous value
ii. Cycle
iii. Time period
iv. Frequency
iv. Amplitude [5M]
- b) Derive expression for relation between phase and line voltages and currents of 3-phase balanced star connection.
6. Draw the constructional diagram of a single phase transformer and explain all the parts. [10M]
- OR**
7. a) Compare Core type & Shell type transformer. [5M]
b) Explain about auto transformer. [5M]
8. Describe the constructional details of D.C machines in detail with neat sketch. [10M]
- OR**
9. a) Define Torque and derive the expression for torque in a D.C. Motor. [5M]
b) What are the losses occur in a D.C Generator? [5M]
10. Explain construction and working principle of three-phase induction motor. [10M]
- OR**
- 11.a) List the starting methods of three-phase induction motor and explain any one of them in details. [5M]
b) A three phase induction motor is wound for 4 poles and is supplied from 50 Hz System. Calculate (i) synchronous speed (ii) speed of the motor when slip is 4% and (iii) Rotor current frequency when the motor runs at 600rpm . [5M]
