

Code No.: EE204ES

R20

H.T.No.

			8	R					
--	--	--	---	---	--	--	--	--	--

CMR ENGINEERING COLLEGE: : HYDERABAD
UGC AUTONOMOUS
I-B.TECH-II-Semester End Examinations (Supply) - February- 2024
BASIC ELECTRICAL ENGINEERING
(Common for CSM, ECE, AI&DS)

[Time: 3 Hours]

[Max. Marks: 70]

Note: This question paper contains two parts A and B.
Part A is compulsory which carries 20 marks. Answer all questions in Part A.
Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART-A


(20 Marks)

- 1. a) State and Explain Kirchoff's laws. [2M]
- b) State Thevenin's Theorem. [2M]
- c) Define: 1) Cycle 2) Amplitude of an alternating Quantity. [2M]
- d) Derive the expression for RMS Value. [2M]
- e) Draw equivalent circuit diagram of Transformer when quantities referred to primary. [2M]
- f) Define the Regulation of a transformer. [2M]
- g) Explain about types of losses in a DC Machine. [2M]
- h) Explain about back EMF. [2M]
- i) Write the differences between squirrel cage and slip ring induction motors. [2M]
- j) What are the applications of three-phase induction motor? [2M]

PART-B


(50 Marks)

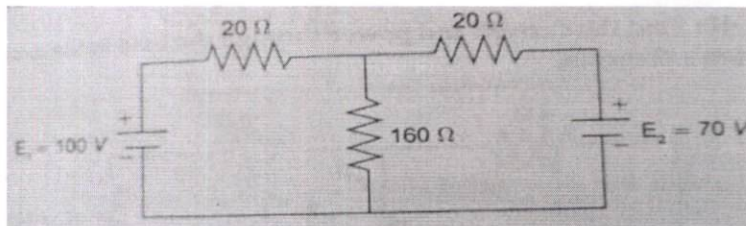- 2. Find current in 160Ω in the given circuit using Norton's theorem. [10M]



OR

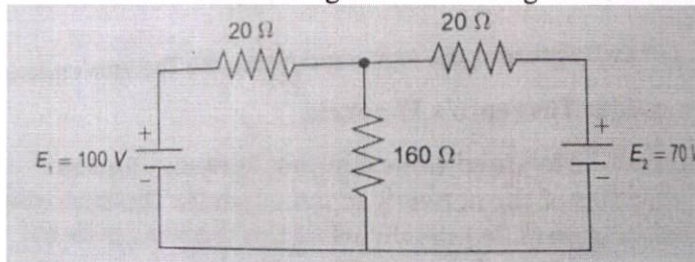- 3. Find current in 160Ω in the given circuit using Thevenin's theorem. [10M]



- 4.a) Explain Single phase AC generation in detail. [5M]
- b) Write about Impedance triangle and Power Triangle. [5M]

OR

- 5. A series circuit consisting of 10 ohms resistor, 100 micro farad capacitance and 10 milli henry Inductance is driven by a 50hz AC voltage source of maximum value 110V. Calculate the equivalent impedance, current in the circuit, power factor. [10M]

- 6.a) Explain in detail Construction, Working Principle of operation of transformer. [5M]
b) Derive EMF Equation of Transformer. [5M]

OR

7. The no load current of a transformer is 5A at 0.3p.f. When supplied at 230V, 50Hz. [10M]
The number of turns on the primary winding is 200. Calculate i) Max. Flux in the core
ii) Magnetizing current. iii) Iron losses in the transformer.

- 8.a) With the help of a neat sketch, Explain the construction and working principle of a [5M]
DC Generator.

- b) A 6 pole lap wound DC Generator has 720 conductors, a flux of 40mWb per pole, is [5M]
driven at 400 RPM. Find the generated EMF.

OR

- 9.a) A 4 pole lap wound DC shunt generator supplies 50 lamps of 100 watts, 200V each. [5M]
The field and armature resistance are 50 Ohms and 0.2 Ohms respectively. Allowing a
brush drop of 1V each brush, calculate the generated EMF

- b) Draw the various characteristics of D C shunt motor. [5M]

- 10.a) Explain the working of a 3-phase induction motor with a neat sketch. [5M]

- b) The stator of a 3-phase, 4 pole induction motor is connected to a 50Hz supply. The [5M]
rotor runs at 1455 rev/min at full load. Determine (i) Synchronous speed and
(ii) Slip at full load.

OR

11. Explain the construction and working of synchronous generator. [10M]
