

Code No.: R22EE204ES

R22

H.T.No.

8

R

CMR ENGINEERING COLLEGE: : HYDERABAD

UGC AUTONOMOUS

I-B.TECH-II-Semester End Examinations (Supply) - February- 2024

BASIC ELECTRICAL ENGINEERING

(Common for ECE, CSE, IT)

[Time: 3 Hours]

[Max. Marks: 60]

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 10 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART-A


(10 Marks)

1. a) What are the different types of electrical circuit elements? [1M]
- b) State KCL. [1M]
- c) Define RMS value of alternating quantity. [1M]
- d) Define resonance. What is the condition for series resonance? [1M]
- e) What is an Auto-Transformer? [1M]
- f) Define the Efficiency of a transformer. [1M]
- g) What are the essential parts of DC Machines? [1M]
- h) What are the losses which occur in DC generator? [1M]
- i) Define slip of a three-phase induction motor. [1M]
- j) What are different types of 3- phase induction motor? [1M]

PART-B

(50 Marks)

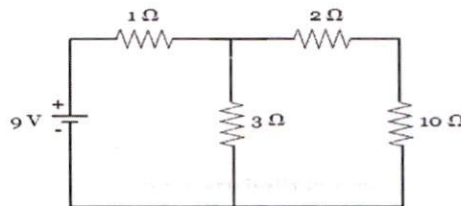- 2.a) State and explain Superposition theorem. [5M]
- b) Find the current through 10 ohms resistance in the given network by using Norton's theorem. [5M]



[5M]

OR

- 3.a) Derive the transient response of an series RL circuit with dc excitation. [5M]
 - b) State and explain Kirchhoff's voltage law with an example. [5M]
4. Derive the expression for Average value, RMS value, form factor and peak factor of sinusoidal waveform $v(t) = V_m \sin \omega t$. [10M]

OR

- 5.a) Derive an expression for resonant frequency of R-L-C series circuit excited by AC source. [5M]
- b) Write the relationship between Phase and Line voltages, currents in star & Delta connected balanced three phase load. [5M]

6. Explain about constructional details and working principle of single phase Transformer. [10M]

OR

7. Draw and explain the equivalent circuit diagram of single phase transformer. [10M]

8. Explain about working principle and constructional details of DC Generator. [10M]

OR

9.a) Derive the Torque equation of DC Motor. [5M]

b) Explain the different types of DC Motors with neat diagrams. [5M]

10. Explain the constructional details and working principle of operation of three phase induction motor. [10M]

OR

11.a) Explain constructional details of synchronous generator. [5M]

b) Explain the various losses occurred in 3-phase induction motor. [5M]
