

Code No.: EC404PC

R20

H.T.No.

8

R

**CMR ENGINEERING COLLEGE: : HYDERABAD**  
**UGC AUTONOMOUS**  
**II-B.TECH-II-Semester End Examinations (Supply) - July - 2024**  
**ELECTRONIC CIRCUIT ANALYSIS**  
**(ECE)**

[Time: 3 Hours]

[Max. Marks: 70]

**Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 20 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

**PART-A**

**(20 Marks)**

1. a) Define distortion in amplifiers. [2M]
- b) List out different types of coupling used in multistage amplifiers. [2M]
- c) What are the types of negative feedback? [2M]
- d) What are the advantages of negative feedback? [2M]
- e) State Barkhausen criterion for Oscillations. [2M]
- f) List out the types of oscillators. [2M]
- g) What are the different types of Tuned Amplifiers? [2M]
- h) What is Heat sink and explain its advantages? [2M]
- i) What are the features of time base signals? [2M]
- j) What are the applications of monostable multivibrator? [2M]

**PART-B**

**(50 Marks)**

2. Explain various methods used for coupling in multistage amplifiers. [10M]
- OR**
3. Derive the expressions for higher and lower cut-off frequency of a multistage amplifier. [10M]
4. Compare voltage series, voltage shunt, current series and current shunt feedback amplifiers with respect to input resistance and output resistance. [10M]
- OR**
5. Draw the circuit of a voltage series feedback circuit and derive its input and output resistances. [10M]
6. Derive the expression for frequency of oscillations of RC-phase shift oscillator. [10M]
- OR**
7. In a Hartley oscillator, if  $L_1=0.2\text{mH}$ ,  $L_2=0.3\text{mH}$  and  $C=0.003 \mu\text{F}$ , calculate the frequency of oscillation. [10M]
8. Explain the operation of a class B push-pull power amplifier and derive its conversion efficiency and list out its advantages and disadvantages. [10M]
- OR**
9. Explain the classification of tuned amplifier. [10M]
10. Draw and explain the working of Bistable Multivibrator. [10M]
- OR**
11. Explain the operation of Transistor Miller time base generator circuit with neat diagram. [10M]

\*\*\*\*\*