

03/02/25

Code No.: R22EE204ES

R22

H.T.No.

		8	R						
--	--	---	---	--	--	--	--	--	--

CMR ENGINEERING COLLEGE:: HYDERABAD
UGC AUTONOMOUS

I-B.TECH-II-Semester End Examinations (Supply) - January- 2025

BASIC ELECTRICAL ENGINEERING

(Common for ECE, CSE, IT)

[Time: 3 Hours]

[Max. Marks: 60]

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 10 marks. Answer all questions in Part A.


Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART-A**(10 Marks)**

1. a) State KVL. [1M]
- b) What are the various types of current sources? [1M]
- c) Define R.M.S value of a sinusoidal quantity. [1M]
- d) What is power factor? [1M]
- e) Define turns ratio of a transformer. [1M]
- f) What is Ideal transformer? [1M]
- g) Why is yoke required in a DC machine? [1M]
- h) What is the significance of back emf? [1M]
- i) Give any one application of 3-phase Induction motor. [1M]
- j) Define slip speed of 3-phase Induction motor. [1M]

PART-B**(50 Marks)**

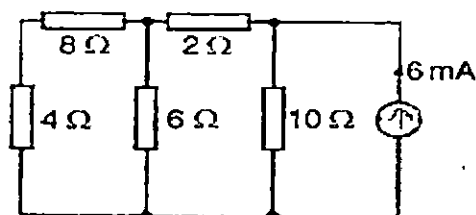2. a) State and explain Norton' theorem. [5M]
 - b) Give the V-I relationship for R, L and C elements. [5M]
- OR**
- 3.a) State and explain Thevenin's theorem. [5M]
 - b) Determine the current flowing in each resistance of the network shown in figure below. [5M]



- 4.a) Obtain an expression for resonant frequency of a series R-L-C circuit excited by an alternating Voltage of variable frequency and constant voltage. [6M]
- b) A series R-L circuit having a resistance of 4Ω and 3Ω inductive reactance is fed by 200 V, 1- ϕ supply. Find current drawn by the circuit. [4M]

OR

5. Three coils each having resistance 3Ω and inductive reactance 4Ω are connected in star to a 440 V, 3-phase supply. Calculate (i) the line and phase voltages and (ii) the phase and line currents. [10M]
6. a) Explain the working principle of single phase transformer. [5M]
b) Draw the equivalent circuit of a transformer when referred to primary from the fundamentals. [5M]

OR

7. a) Explain different losses of a transformer. [5M]
b) A 100-kVA, 3300/400-V, 50 Hz, 1-phase transformer has 110 turns on the secondary. Calculate the approximate values of primary and secondary full-load currents, the maximum value of flux in the core and the number of primary turns. [5M]
8. a) Explain the working principle of a d.c generator. [5M]
b) A 4-pole lap wound generator has 250 conductors on armature. It is driven by a prime mover at a constant speed of 800 rpm. If the flux per pole is 0.2 Wb, Calculate the generated emf? [5M]

OR

9. a) Derive an expression for torque developed by d.c motor. [6M]
b) Draw the torque vs. speed characteristics of all d.c motors [4M]
10. a) A 3-phase, 50 Hz, 6 pole 3-ph induction motor has full load slip of 3 %. Find (i) synchronous speed (ii) motor speed. [6M]
b) Explain the torque-speed characteristics of 3-phase Induction motor? [4M]

OR

11. Explain the constructional details and working principle of synchronous generator. [10M]
