

**CMR ENGINEERING COLLEGE: : HYDERABAD**  
**UGC AUTONOMOUS**

**II-B.TECH-I-Semester End Examinations (Regular) - December- 2024**  
**NETWORK ANALYSIS AND SYNTHESIS**  
**(ECE)**

[Time: 3 Hours]

[Max. Marks: 60]

**Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 10 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

**PART-A****(10 Marks)**

1. a) How many closed paths are available in a tree? [1M]
- b) Define coefficient of coupling. [1M]
- c) What is the time constant of a series RC circuit? [1M]
- d) What do you mean by overdamped and under damped? [1M]
- e) What is driving point function? [1M]
- f) Define characteristic impedance. [1M]
- g) List any two applications of band pass filter. [1M]
- h) Draw the basic configuration of symmetrical lattice network. [1M]
- i) What is Hurwitz polynomial? [1M]
- j) Define positive real function. [1M]

**PART-B****(50 Marks)**

2. In the graph shown in Figure(1), the ideal voltage source  $e = 1V$ . For the remaining branches each has a resistance of  $1 \Omega$  with O as the reference. Obtain the node voltage  $e_1$ ,  $e_2$  and  $e_3$  using network topology. [10M]

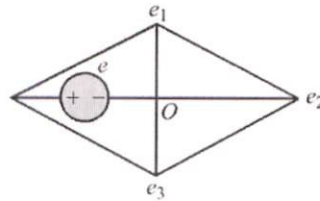


Fig 1.

**OR**

- 3.a) Explain dot convention for coupled circuits. [5M]
  - b) Explain incidence matrix, Tie-set matrix and cut-set matrix. [5M]
  4. Discuss the transient analysis of RLC series circuit excited by D.C. voltage. [10M]
- OR**
- 5.a) A sinusoidal voltage  $v(t) = 20 \sin(75t)$  is applied suddenly to a series RL circuit with  $R = 20\Omega$  and  $L = 4 H$ . Find the time instant at which transient current becomes zero. [6M]
  - b) Define the quality factor. What is its significance? [4M]

6. Find the Z- parameters for the following circuit.

[10M]

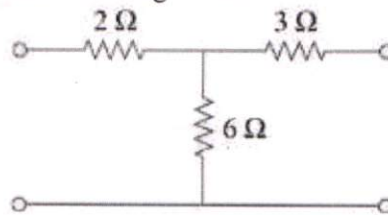


Fig 2

**OR**

- 7.a) Explain the concept of poles, zeros, their significance and necessary conditions for driving point functions and transfer functions? [5M]

- b) Design  $\Pi$ - attenuator with  $50 \Omega$  characteristic impedance and attenuation of 6 dB. [5M]

8. Design an m-derived LPF (T- and  $\pi$ -Section) having a design impedance of  $500 \Omega$  and cut-off frequency 1500 Hz and an infinite attenuation frequency of 2000 Hz [10M]

**OR**

9. Derive the equation of characteristic impedance and attenuation constant of a symmetrical T network. [10M]

- 10.a) What are the properties of LC driving point functions? [4M]

- b) Test the following polynomial are Hurwitz [6M]

i)  $P(S) = S^3 + 4S^2 + 5S + 2$       ii)  $P(S) = S^4 + S^3 + S^2 + 2S + 12$

**OR**

11. The driving point impedance of a one-port reactive network is given by [10M]

$$Z(S) = \frac{5(S^2 + 4)(S^2 + 25)}{S(S^2 + 16)}$$

Obtain Foster I & II networks.

\*\*\*\*\*