

Code No: 09A30203

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY, HYDERABAD**B.Tech II Year I Semester Examinations, June/July-2014****ELECTRONIC DEVICES AND CIRCUITS****(Common to EEE, ECE, CSE, EIE, BME, IT, MCT, ETM, ECOMPE, ICE)****Time: 3 hours****Max. Marks: 75**

Answer any five questions
All questions carry equal marks

- 1.a) Two identical Si diodes are connected back-to-back with 10V battery. Calculate potential difference between each diode.
- b) Derive the expression for transition capacitance $\left(C_T = \frac{\epsilon A}{w} \right)$ of a junction diode.
- 2.a) Define the following terms and derive the equations with respect to half-wave rectifier:
i) Ripple factor
ii) Peak inverse voltage
iii) % Regulation.
- b) A HWR circuit supplies 100mA DC current to a 250Ω load. Find the DC output voltage, PIV rating of a diode and the r.m.s. voltage for the transformer supplying the rectifier.
- 3.a) With the help of a neat diagram explain different current components in an NPN bipolar junction transistor.
- b) With reference to bipolar junction transistors, define the following terms and explain.
i) Emitter efficiency
ii) Base Transportation factor.
iii) Large signal current gain.
- 4.a) What do you mean by the quiescent point of transistor amplifier?
b) What is a load line? Explain its significance.
c) Find the Q-point of self-bias transistor circuit with the following specifications: $V_{CC} = 22.5V$, $R_L = 5.6k\Omega$, $R_C = 1k\Omega$, $R_1 = 90k\Omega$, $R_2 = 10k\Omega$, $V_{BE} = 0.7V$ and $\beta = 55$. Assume $I_B \gg I_{CO}$.
- 5.a) Derive the expressions for A_I , A_V , R_i , R_o for CE Transistor configuration.
b) For the emitter follower with $R_S = 0.5K$, $R_L = 50K$, $h_{fe} = -50$, $h_{ie} = 1K$, $h_{oe} = 25\mu A/V$, $h_{re} = 1$. Calculate A_V , A_I , Z_i and Z_o .
- 6.a) With neat sketches, necessary equations explain the drain and transfer characteristics of MOSFET in enhancement mode.
b) Define the FET parameters and derive relation between them.
c) Why is a JFET is called Unipolar and voltage controlled device.

- 7.a) Draw the small-signal model of common source FET amplifier. Derive expressions for voltage gain and output resistance.
- b) Give the UJT symbol and simplified equivalent circuit with external resistors included. Describe its negative-resistance nature, with the help of V-I characteristics.
8. Explain the principle of operation of the following devices:
- a) Schottky Barrier diode
- b) Tunnel diode through Energy band diagrams.

---oo0oo---

Handwritten watermark text "H5" is visible in the center of the page.