

Code No: 53015

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year I Semester Examinations, March - 2017

ELECTRICAL AND ELECTRONICS ENGINEERING


(Common to PTM, AME, CE, ME)

Time: 3 hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

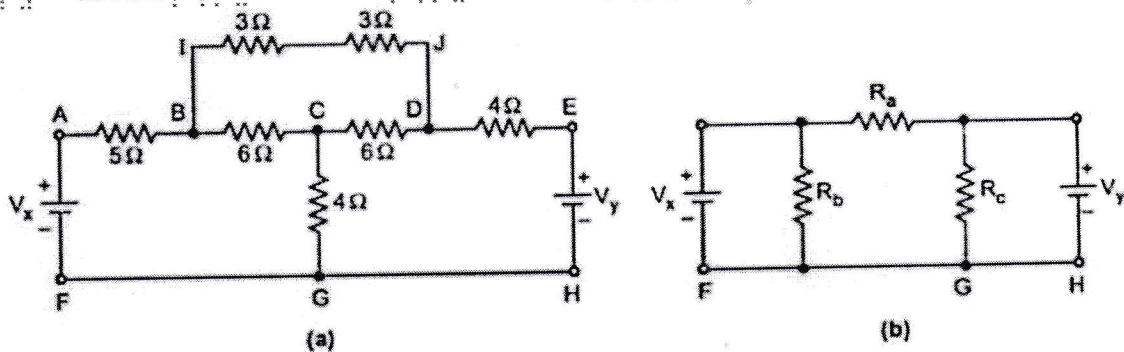- 1.a) A circuit is shown in figure a. Using delta-star analysis, reduce it to the circuit as shown in the figure b. Find the values of R_a , R_b , R_c in the equivalent form of the circuit.



- b) A 20V battery with an internal resistance of 5 ohms is connected to a resistor of x ohms. If an additional resistance of 6. is connected across the battery, find the value of x , so that the external power supplied by the battery remain the same. [7+8]

- 2.a) Discuss the working principle of DC generator.

- b) A DC generator has an armature emf of 100 V when the useful flux per pole is 20 m Wb, and the speed is 800 rpm. Calculate the generated emf (i) with the same flux and a speed of 1000 rpm, (ii) with a flux per pole of 24 m Wb and a speed of 900 rpm. [7+8]

3. Calculate efficiency and regulation at full load, 0.8 p.f. lagging for a 10 kVA, 1phase, 50Hz, 500/250 V transformer gave following results:

- a) OC test (LV) side: 250V, 3.0A, 200W
b) SC test (LV) side: 15 V, 30A, 300 W. [7+8]

- 4.a) Sketch the torque slip characteristic of a 3-ph induction motor indicating there in the starting torque, maximum torque and the operating region. How do starting and maximum torques vary with the rotor resistance.

- b) Find the no load phase and line voltage of a star connected 3 ph, 6 pole alternator which runs at 1200 rpm, having flux per pole of 0.1 Wb sinusoidally distributed. Its stator has 54-slots having double layer winding. Each coil has 8 turns and the coil is chorded by 1 slot. [7+8]

5.a) Explain the constructional features of the following type instruments Moving Coil.

b) With the help of neat sketches explain the working of moving iron Instrument.

[8+7]

6.a) What is ripple factor and obtain the ripple factor for single phase full wave Rectifier?

b) Describe the action of pn junction diode under forward and reverse bias conditions.

[8+7]

7.a) Classify and Explain the types of Feedback amplifiers.

b) Write short notes on: (i) Transistor as an amplifier, (ii) SCR characteristics and applications.

[7+8]

8.a) Explain how the applied voltage wave is displayed on the screen of a cathode ray tube. Sketch the same.

b) Explain with block diagram the various parts of a CRT. What extra components are needed to make it a CRO? Explain how would you measure frequency using a CRO.

[7+8]

---ooOoo---