

Code No: 09A30303

R09

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY, HYDERABAD
B.Tech II Year I Semester Examinations, November/December-2013

Electrical and Electronics Engineering
(Common to CE, ME, AME, PTE, CEE, MSNT)

Time: 3 hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

- 1.a) Three resistances of R ohms each are connected in a delta. Transform it to an equivalent star with resistances R_1 , R_2 and R_3 in terms of R .
b) By applying Kirchoff's law, find the current through all the elements in the circuit shown in the Figure1. [15]

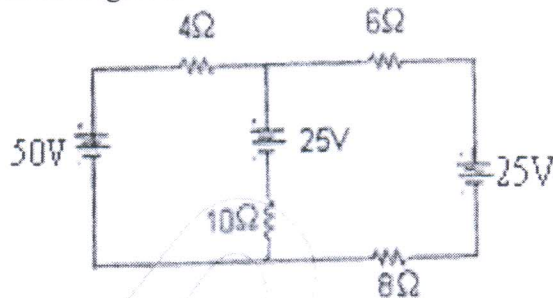


Figure 1

- 2.a) Derive the emf equation of a DC generator.
b) Explain the operation of a DC motor. Mention the different types of DC motors. [15]
- 3.a) Explain the working principle of a single phase transformer with a phasor diagram.
b) A 50KVA single phase transformer has a full load primary current of 250A and total resistance referred to primary is 0.006Ω . If the iron losses are 200 W. Find the efficiency on full load and half load at UPF. [15]
- 4.a) Discuss how regulation of an alternator can be determined by synchronous impedance method.
b) A 3-phase induction motor is wound for 4 poles and is supplied from 50 Hz system. Calculate
(i) the synchronous speed, (ii) the speed of the motor when slip is 4% and
(iii) the rotor current frequency when the motor runs at 600 r.p.m. [15]
- 5.a) With the help of neat diagram, explain the working of Moving Iron instruments.
b) Write the advantages and disadvantages of PMMC instruments. [15]
- 6.a) With a neat circuit diagram, explain the operation of bridge type full wave rectifier.
b) The applied input a.c. power to a half-wave rectifier is 100 watts. The d.c. output power obtained is 40 watts. i) What is the rectifier efficiency? ii) What happens to remaining 60 watts? [15]

- 7.a) Prove that the transistor acts as an amplifier with suitable circuit diagram.
b) Explain the function of SCR with its V-I characteristics. [15]
- 8.a) Derive the expression for magnetic deflection sensitivity of a Cathode ray tube.
b) Discuss how voltage, current and frequency are measured with CRO. [15]

---oo0oo---

8R