

R09

Code No: 09A50201

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY, HYDERABAD

B. Tech III Year I Semester Examinations, November/December-2013

IC APPLICATIONS

(Common to EEE, ECE, ETM)

Time: 3 hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

- 1.a) List and compare ideal and practical characteristics of an Op-Amp.
- b) What are the differences between the inverting and non-inverting terminals of Op-Amp? What do you mean by the term virtual ground? [7+8]
- 2.a) Explain the working of an ideal active differentiator.
- b) Draw and explain the operation of an op-amp as an integrator. [7+8]
- 3.a) Draw the circuit of RC phase-shift oscillator using op-amp. Derive expression for its frequency of oscillations?
- b) Design a wide band pass filter with $f_L=200\text{Hz}$, $f_H=1\text{kHz}$, and a pass band gain=4 using Op-Amps. [8+7]
- 4.a) Explain the operation of 555 timer based Monostable multivibrator with functional diagram?
- b) Define
 - i) Lock-in range
 - ii) Capture range
 - iii) Pull-in time. [9+6]
- 5.a) Explain the operation of weighted resistor DAC with neat circuit diagram
- b) List out different types of A/D converters. [10+5]
- 6.a) Sketch CMOS NAND gate and explain its working.
- b) What is meant by Tri-static logic? Draw the circuit of Tri-state TTL logic and explain its functions. [7+8]
- 7.a) Explain how to use multiplexer as a logic function generator
- b) Explain 4-bit parallel binary subtractor circuit using 2's Complement system. [7+8]
- 8.a) Using the method of flip-flop conversion carry out the following conversions.
 - i) S-R to T
 - ii) J-K to D
- b) Describe the operation of an asynchronous decade counter [8+7]
