

Time: 3 hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

- 1.a) Differentiate between ideal sources and practical sources.
b) Find the equivalent voltage and current source representation of the following network across AB (figure 1). [7+8]

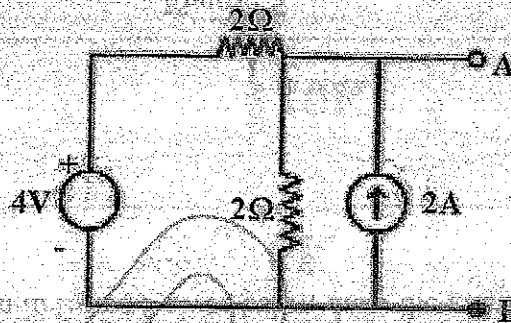


Figure: 1

- 2.a) Find the node voltages V_1 , V_2 and V_3 in the network of figure 2, and find the current I_x .

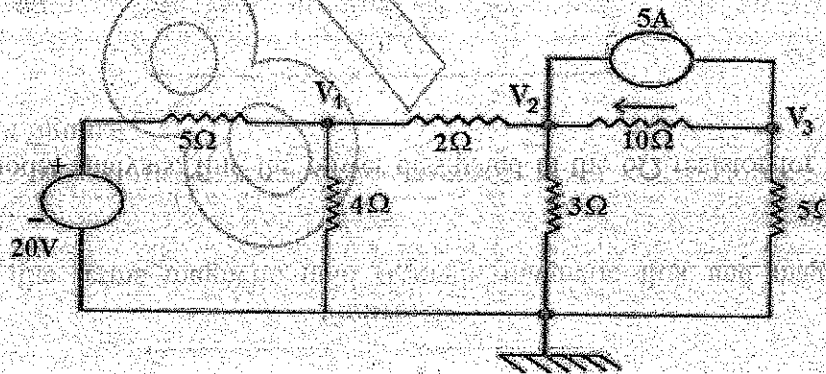


Figure: 2

- b) Two resistances when they are in series have an equivalent resistance of 9 ohms and when connected in parallel have an equivalent resistance of 2 ohms. Find the resistance and the ratio of the voltage and current sharing between these elements if supply voltage is 100V. [7+8]
- 3.a) Derive the expression for power in 1- ϕ A.C. Circuits.
b) A 50Hz sinusoidal voltage applied to a single phase circuit has its RMS value of 200V its value at $t=0$ is 28.3 volt positive. The current drawn by the circuit is 5A RMS and lags behind the voltage by one sixth of a cycle. Write the expressions for instantaneous values of voltage and current. [7+8]

4 a) A RLC series circuit consists of $R=50 \Omega$, $L=0.16H$ and $C=4\mu F$. Calculate resonant frequency, quality factor, band width and half power frequencies.

b) For the RLC series circuit $R=5\Omega$, $L=0.03H$, $C=100 \mu F$. Determine the Frequency at which the circuit resonates. Also find the quality factor, voltage across the inductance, voltage across capacitance, at resonance.

[7+8]

5 a) The combined inductance of two coils connected in series are $0.6 H$ and $0.1 H$ in series aiding and Series opposing connections. If the self inductance of each coil is $0.2H$, find the coefficient of coupling.

b) In the network shown in Figure 3, $L_1=1H$, $L_2=2H$, $M=1.2 H$. Assuming the inductance coils to be ideal find the amount of energy stored after 0.1 sec of the circuit connected to a d.c. source of $10V$.

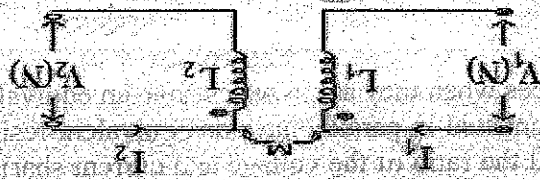


Figure: 3

c) Explain the terms magnetic field strength, magnetic flux and magnetic flux density.

6 a) Using nodal analysis, find the power dissipated in the 6Ω resistor for the circuit shown in figure 4.

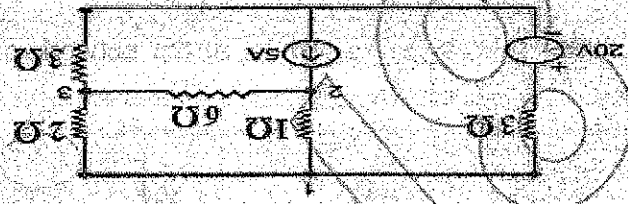


Figure: 4

b) For the circuit shown in figure 5 given below draw the graph and use.

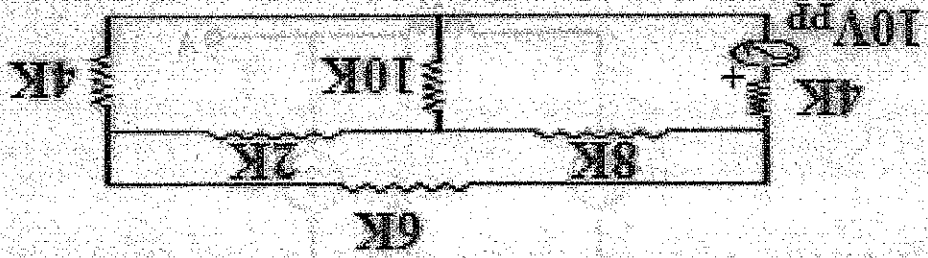


Figure: 5

7 a) State and explain Thevenin's and Norton's theorems.

b) Calculate the current I shown in figure 6 using Millman's theorem.

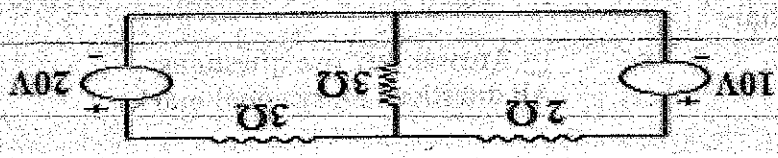


Figure: 6

[7+8]

- 8.a) State and explain Tellegen's Theorem.
 b) In the network shown in the Figure 7. Find the value of Z_L so that the power transfer from the source is maximum. Also find P_{max} . [7+8]

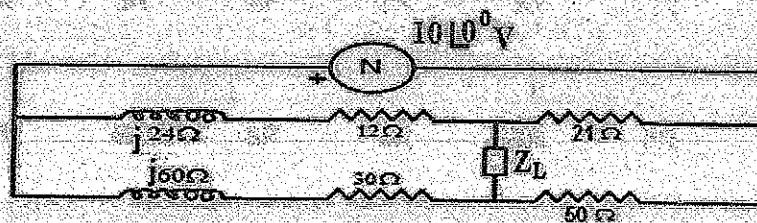


Figure: 7

--00000--

8R

