

**R13**

Code No: 114AF

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year II Semester Examinations, October/November - 2016

DIGITAL DESIGN USING VERILOG HDL

(Electronics and Communication Engineering)

Time: 3 Hours

Max. Marks: 75

**Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

**PART - A****(25 Marks)**

- 1.a) Define Keywords and Identifiers. [2]
- b) Define parameters and memory operators. [3]
- c) Define strengths and content resolution. [2]
- d) What is continuous assignment structure? [3]
- e) Explain assignments with delays. [2]
- f) Draw a simulation flow chart. [3]
- g) Explain the operation of PMOS switch. [2]
- h) Explain basic transistor switches. [3]
- i) Explain capacitive model. [2]
- j) What is sequential circuit testing? [3]

**PART - B****(50 Marks)**

2. Explain with examples about:  
a) Display tasks    b) Strobe tasks    c) Monitor tasks. [3+3+4]  
**OR**
- 3.a) Using example, explain about concurrent and procedural statement with syntaxes.  
b) Explain the components of a Verilog module with block diagram. [5+5]
- 4.a) Write a Verilog code for tri-state devices.  
b) Explain clocked RS flip-flop Verilog module and test bench. [5+5]  
**OR**
- 5.a) Design a Verilog module of a 4-bit bus switcher at the data flow level.  
b) Explain about operator priority with examples. [5+5]
- 6.a) Explain blocking and non-blocking statement with examples.  
b) Write Verilog code using case statement for any one example. [5+5]  
**OR**
- 7.a) Explain event construct in a module.  
b) Explain stratified event queue. [5+5]

- 8.a) Design Verilog module for CMOS flip-flop. [5+5]  
b) Explain about module paths.

**OR**

- 9.a) Explain overriding parameters. [5+5]  
b) Design Verilog module using path delay.

- 10.a) What are the various sequential memory storage models? Explain in detail.  
b) How the memory initialization carried out in Verilog? Explain with the help of an example. [5+5]

**OR**

- 11.a) With the help of an example explain about the resetting sequence of controller.  
b) Write a test bench for moore detector to control the delay. [5+5]

---ooOoo---