

R15

Code No: 123CT

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**B.Tech II Year I Semester Examinations, November/December - 2016****DIGITAL LOGIC DESIGN****(Computer Science and Engineering)****Time: 3 Hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

PART-A**(25 Marks)**

- 1.a) Explain duality theorem with example. [2]
- b) Convert following hexadecimal number to decimal.
 - i) $F28_{16}$ ii) $BC2_{16}$. [3]
- c) Implement Ex-NOR gate using only NAND gates. [2]
- d) Obtain the prime implicants for given Boolean expression using K-map.
 $f(A, B, C) = \sum(1, 3, 6, 7)$. [3]
- e) What is code converter? [2]
- f) Explain the analysis procedure for combinational circuit. [3]
- g) Explain clear and preset inputs. [2]
- h) What is race around condition? [3]
- i) Explain the role of Cache Memory in sequential circuits. [2]
- j) Compare ROM and RAM. [3]

PART-B**(50 Marks)**

- 2.a) Using 2's complement perform $(42)_{10} - (68)_{10}$.
 - b) Implement the following Boolean function with NOR-NOR logic
 $F(A,B,C) = \pi M(0,2,4,5,6)$. [5+5]
- OR**
- 3.a) What is the specialty of unit-distance code? State where they are used.
 - b) Give the Boolean expressions used for following gates
 - i) AND ii) NOR iii) EX-OR iv) OR v) EX-NOR. [5+5]
4. Reduce the following functions using K-map techniques.
- a) $f(A, B, C, D, E) = \sum m(1, 4, 8, 10, 11, 20, 22, 24, 25, 26) + d(0, 12, 16, 17)$
 - b) $f(A, B, C, D) = \pi M(4, 5, 6, 7, 8, 12, 13) + d(1, 15)$. [5+5]

OR

- 5.a) Using K-map obtain the minimal sum of products and the minimal product of sums from of the function $f(a,b,c,d) = \sum m(1, 2, 3, 5, 6, 7, 8, 13)$.
 - b) Explain about essential prime implicants. [5+5]
6. Design the full adder circuit using decoder and de-multiplexer. [10]

OR

- 7.a) Write a short note on priority encoder.
- b) What is decoder? [5+5]

- 8.a) Compare combinational circuits and sequential circuits.
b) Explain the clocked JK flip-flop with truth table.

[5+5]

OR

9. Draw and explain the working of following flip-flops:
a) RS b) D.

[5+5]

- 10.a) Draw and explain the block diagram of PLA.
b) Explain address and data bus in digital electronics.

[5+5]

OR

11. Implement the following function using a PROM.

a) $F(A, B, C, D) = \sum m(1, 9, 12, 15)$

b) $G(A, B, C, D) = \sum m(0, 1, 2, 3, 4, 5, 7, 8, 10, 11, 12, 13, 14, 15)$.

[5+5]

---oo0oo---